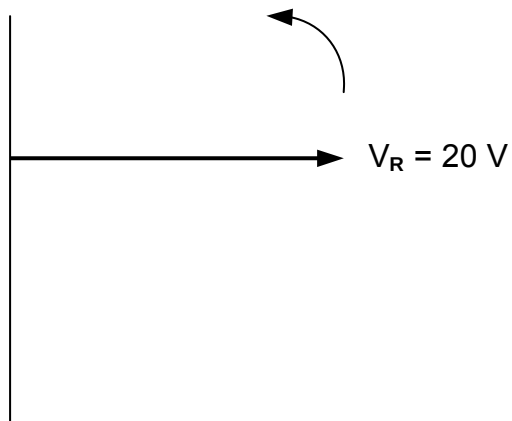


CENTRE NUMBER:									
----------------	--	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:														
---------------------	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET**QUESTION 2: RLC CIRCUITS**

2.1.1


**FIGURE 2.1.1**Transfer mark to
answer book

--	--

MOD

(2)

2.2.4

 **FIGURE 2.2.4**Transfer mark to
answer book

--	--

MOD

(5)

CENTRE NUMBER:

EXAMINATION NUMBER:

ANSWER SHEET

QUESTION 4: SWITCHING CIRCUITS

4.3.2

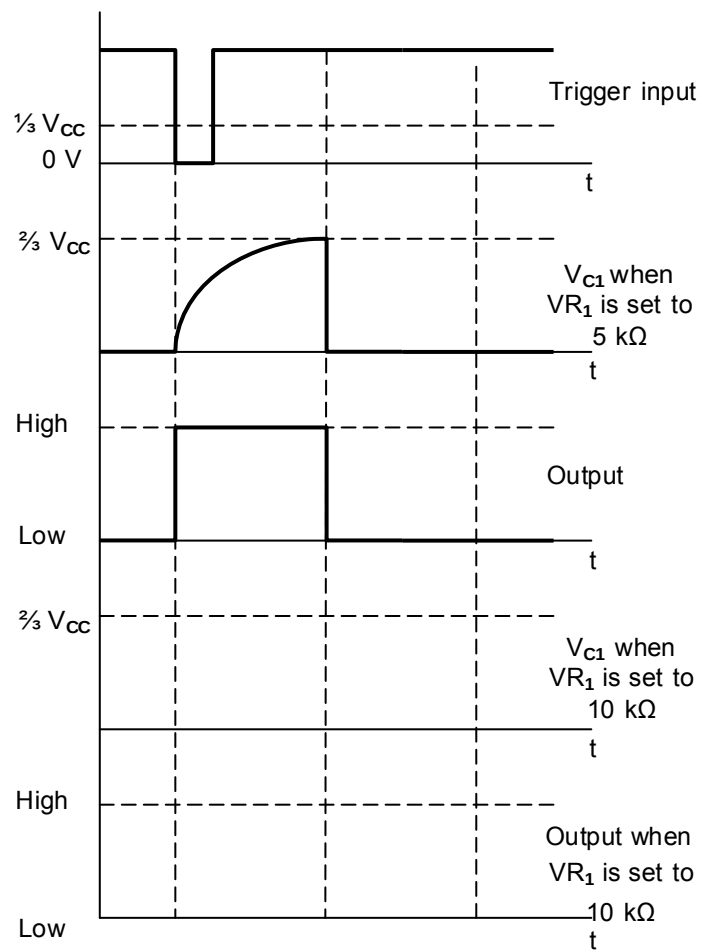


FIGURE 4.3.2

Transfer mark to
answer book


MOD

(4)



CENTRE NUMBER:**EXAMINATION NUMBER:****ANSWER SHEET**

4.4.2

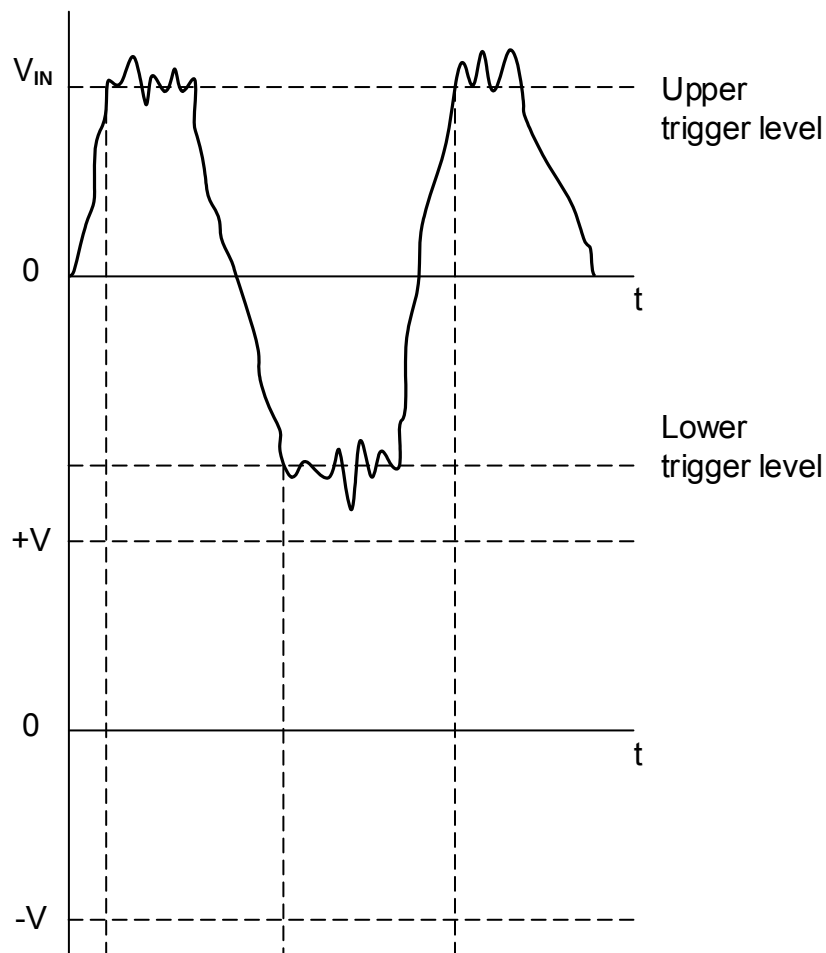**FIGURE 4.4.2**Transfer mark to
answer book

MOD

(4)

CENTRE NUMBER:


--	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET

4.6.2

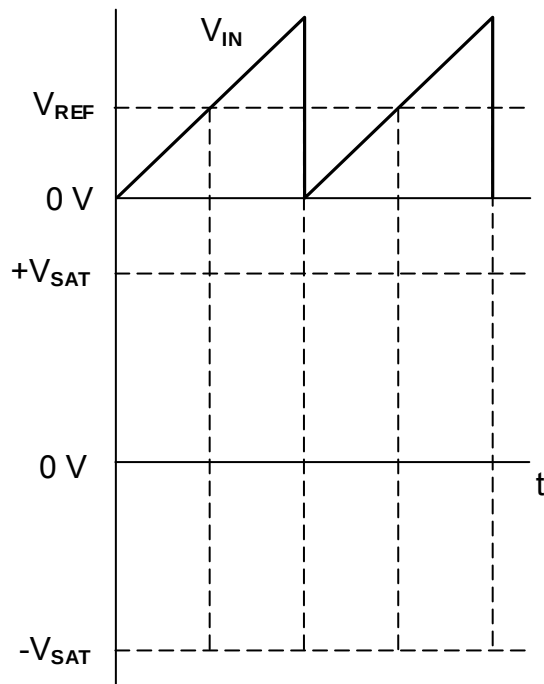**FIGURE 4.6.2**Transfer mark to
answer book

--	--

MOD

(4)



CENTRE NUMBER:

--	--	--	--	--	--	--	--	--	--

EXAMINATION NUMBER:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ANSWER SHEET

4.8.2

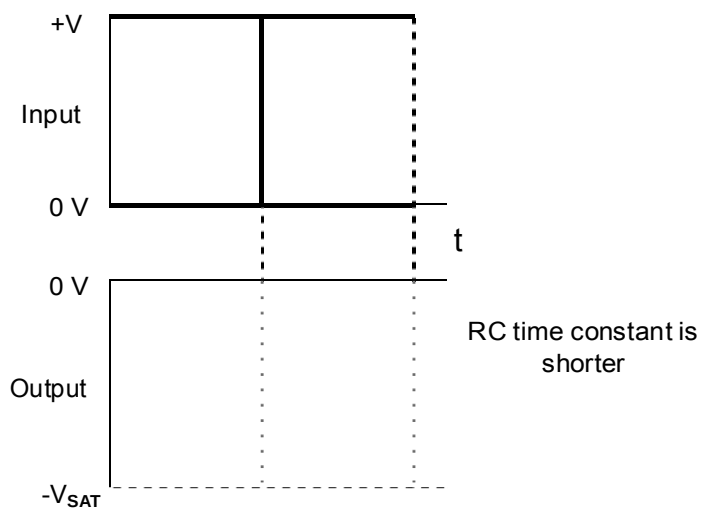


FIGURE 4.8.2

Transfer mark to
answer book

--	--

MOD

(2)

4.8.3

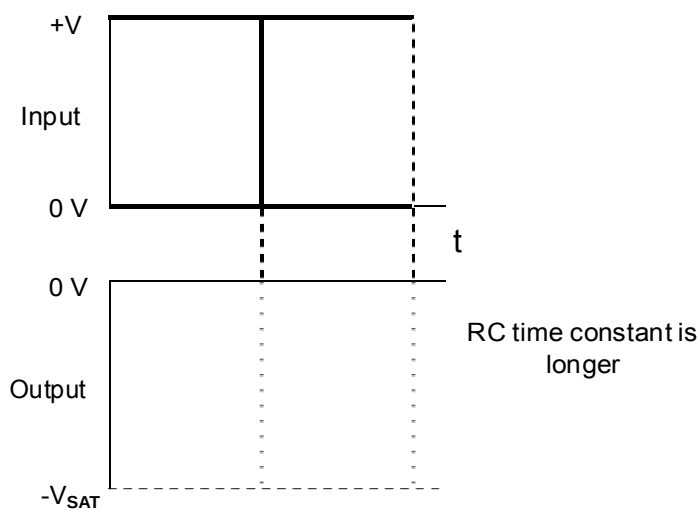


FIGURE 4.8.3

Transfer mark to
answer book

--	--

MOD

(2)

